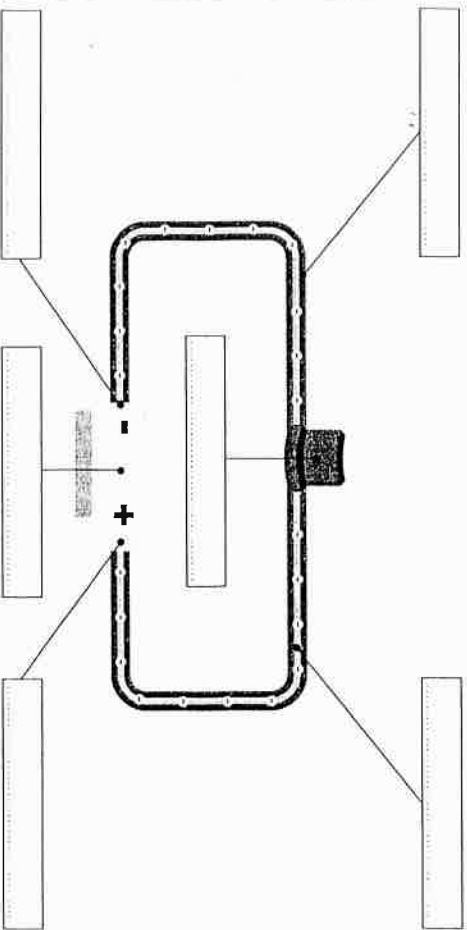


Name: _____
Date: September 7, 2016

LABEL IT

Using terms from the word bank, label the components of the electrical circuit.

NEGATIVE TERMINAL **POSITIVE TERMINAL** **POWER SOURCE**
LOAD **RUBBER INSULATION** **COPPER WIRE**



THINK ABOUT IT

In the previous exercise, which component could you remove, and still have a functioning circuit? In general, why would removing that component be a bad idea?

Name: _____
Date: September 7, 2016

DEFINE

Can you explain the terms below in your own words?

ELECTRIC CIRCUIT:

ROUTE (VERB):

ELECTRONS:

STATIC ELECTRICITY:

CURRENT (IN ELECTRICITY):

COMPONENT:

CONDUCTOR (IN ELECTRICITY):

INSULATOR (IN ELECTRICITY):

Choose an additional term from the movie to define.